# 電工實驗5

第一次實驗 預報

Date: 2024/09/24

Class: 電機四全英班


Group: Group 9

Name: B103105006 胡庭翊

B103015018 劉姵好


#### I. TXLINE 參數設定

#### A. 40 Ohm:

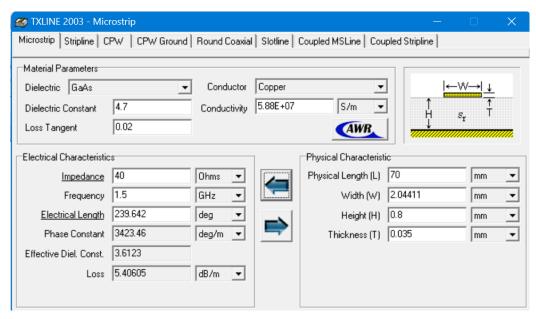

結論: W = 2.04411mm

#### B. 20 Ohm:

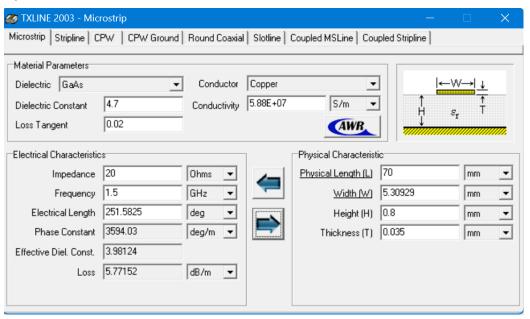

結論:W=5.30929mm

#### II. Libra 的 code

#### A. 40 Ohm 開路

```
DIM
FREQ
     GHZ
RES
     OH
LNG
     MM
ANG
      DEG
IND
      NH
CAP
       PF
CKT
       ER=4.7 H=0.8 T=0.035 RHO=0 RGH=0
MSUB
TAND
             TAND=0.02
MLIN
             2
                     W=2.04411
                                    L=70
         EXP1
DEFIP
      1
FREQ
         4
                   0.01
SWEEP 0
OUT
       DB[S11] GR1
EXP1
      MAG[z1] GR2
EXP1
GRID
                   0.01
RANGE 0 4

GR1 -2 0.5

GR2 -100 1500
                    0.01
                     100
```

#### B. 40Ohm 短路

```
DIM
FREQ
      GHZ
RES
LNG
     MM
ANG
      DEG
IND
      NH
CAP
      PF
CKT
MSUB
      ER=4.7 H=0.8 T=0.035 RHO=0 RGH=0
TAND
             TAND=0.02
             2 W=2.04411
0 R=0
MLIN
                               L=70
RES
      2
DEFIP
             EXP1
FREQ
         4
SWEEP 0
                  0.01
OUT
EXP1
     DB[S11] GR1
EXP1
     MAG[z1] GR2
GRID
      0 4
-2 0.5
RANGE 0
                  0.01
GR1
                  0.01
GR2
      -100 1500
                  100
```

# C. 20Ohm 開路

DIM					
FREQ	GHZ				
RES	OH				
LNG	MM				
ANG	DEG				
IND	NH				
CAP	PF				
CKT					
MSUB	ER=4.7	H=0.8	T=0.035 RHO=0	RGH=0	
TAND		TAND=0.02			
MLIN	1	2	W=2.04411	L=70	
RES	2	0	R=0		
DEF1P	1	EXP1			
FREQ					
SWEEP	0	4	0.01		
OUT					
EXP1	DB[S11]	GR1			
EXP1	MAG[z1]	GR2			
GRID					
RANGE	0	4	0.01		
GR1	-2	0.5	0.01		
GR2	-100	1500	100		


# D. 20Ohm 短路

DIM					
FREQ	GHZ				
RES	OH				
LNG	MM				
ANG	DEG				
IND	NH				
CAP	PF				
CKT					
MSUB	ER=4.7	H=0.8	T=0.035 RHO=0	RGH=0	
TAND		TAND=0.02			
MLIN	1	2	W=5.30929	L=70	
RES	2	0	R=0		
DEFIP	1	EXP1			
FREQ					
SWEEP	0	4	0.01		
OUT					
EXP1	DB[S11]	GR1			
EXP1	MAG[z1]	GR2			
GRID					
RANGE	0	4	0.01		
GR1	-2	0.5	0.01		
GR2	-100	1500	100		


### III.模擬結果

#### A. 40Ohm 開路

### 1. S11

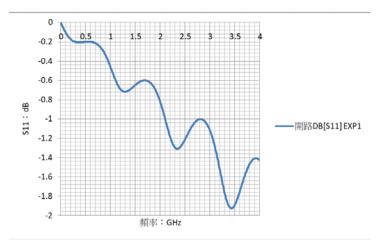


### 2. Z1

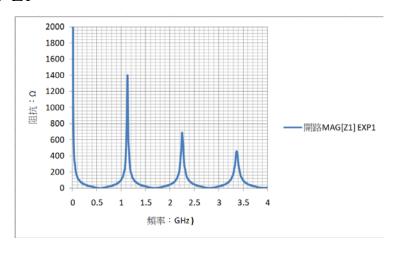


#### B. 40Ohm 短路

#### 1. S11

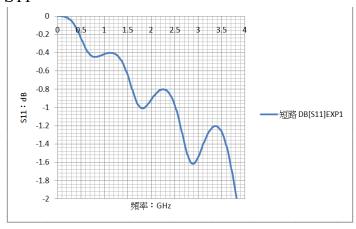

# 2. Z1

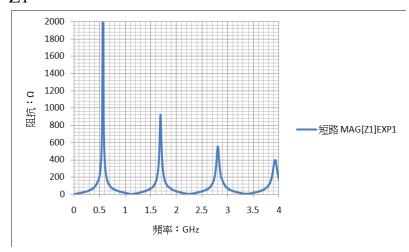


# C. 20Ohm 開路

# 1. S11




### 2. Z1

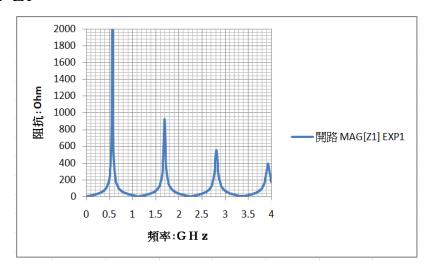

### D. 20Ohm 短路

### 1. S11

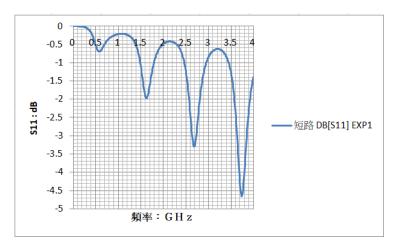

# 2. Z1

