

Digital Lab 3:

Experiment4:

LED Light Control Circuit

Date: 2023/11/09


Class: 電機三全英班

Group: Group 11


Name: B103105006 胡庭翊


I. Block Diagram

Structure:

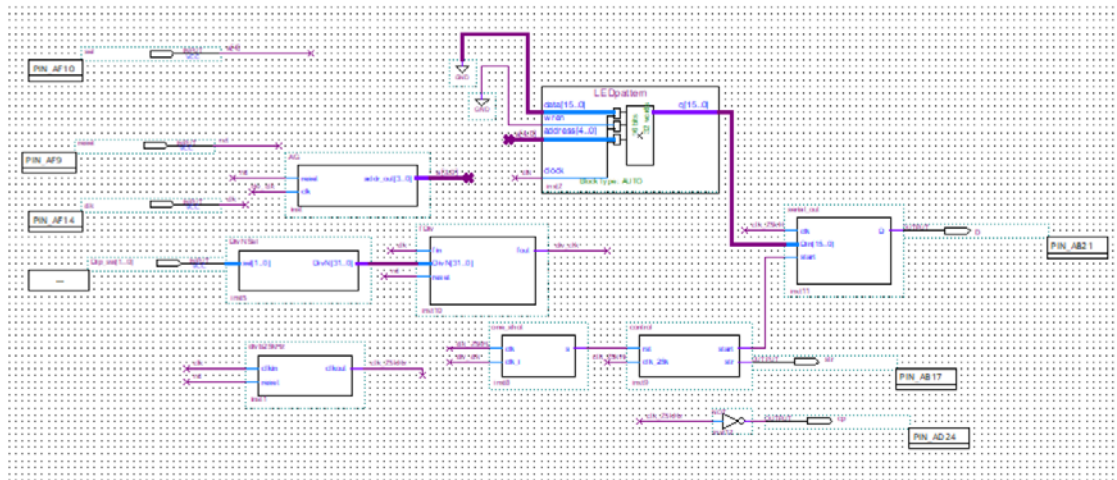

Function:

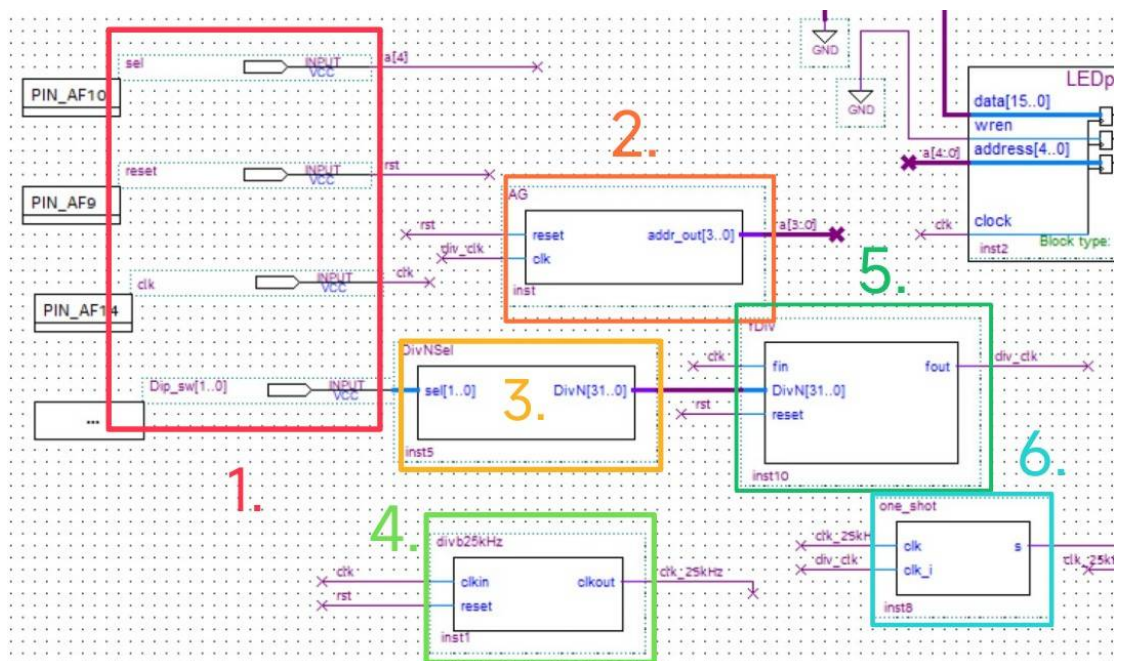

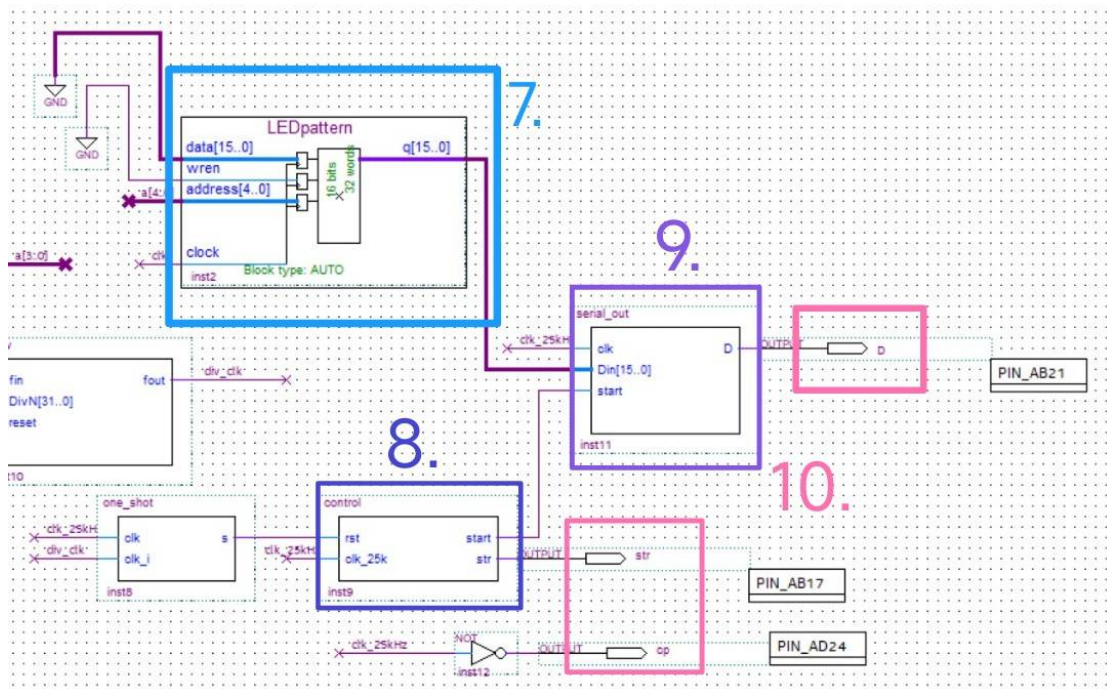

Descriptions:

1. Inputs

Here, to control the circuit, we have one bit of reset, a 50M Hz clock input connected to the FPGA board, a two bit dip switch of speed control for selecting frequency , and a select bit to choose the output pattern mode of the LED which is connected to the memory.

2. Address Generator

Generates the 4-bit address values required for memory. When the "rst" signal is raised, the address is reset to zero, allowing the memory to start outputting data from the beginning.

3. Division Selector

Select the needed frequency corresponding to the 2-bit dip-switch, the possible frequencies that are needed are 2Hz, 4Hz, 6Hz and 8Hz.

4. 25kHz Frequency Divider

Convert 50MHz of the clock on the FPGA board into 25kHz.

5. Frequency Divider 50M/divHz(iHz):

Converts the 50 MHz signal on the board into 2 Hz, 4 Hz, 6 Hz, and 8 Hz signals to control the speed of switching the stored patterns in memory.

6. One Shot

Designed using a state machine, it generates a pulse signal of length 1 clock cycle (25 kHz) after a longer input signal's positive edge trigger.

Transfer the low frequency into an active high frequency circuit module.

7. Memory

Megafunction-generated memory module (16 bits * 32 words) that stores two different LED patterns, as provided in the attached MIF file.

8. Control

Provides the clock signal to the IC. As Serial Out uses a positive-edge trigger, an inverter is applied to the IC's CLOCK (CP) signal to make it negative-edge triggered.

This ensures that data is written to the IC when it's ready, synchronized with the negative edge trigger.

9. Serial Output

When "start" is set to 1, the input 16-bit value is stored in the register.

After "start" becomes 0, on each positive edge of the clock, the highest bit of the register is sequentially sent out to D

10. Outputs

Pins: str, CP, D

Control the latch enable, input clock, and data for each IC separately.

II. Address Generator


A. Verilog Code and Comment

```
1 module AG(reset, clk, addr_out);
2
3 input reset, clk; //input declaration
4 output reg [3:0] addr_out; //4-bit output address
5
6 reg [3:0] count;
7 wire [3:0] _addr_out;
8
9 always@(posedge clk or posedge reset) //when clk or reset is in posedge
10 begin
11     if(reset)
12         count<=7'b0; //when reset goes to 1, assign 7 bits of 0 into count, that is, reset its value
13     else
14         count<=(count>=7'd15)?7'd0:count+1; /*if count reaches to 7'd15, restart its value,
15                                             otherwise, keep counting*/
16     end
17
18 always@(negedge clk) //clk is negedge triggered
19     addr_out<=count; //assign count value to the output
20 endmodule
21
```

 B. Simulation

The address would be generated when either the clock or reset is in posedge.

The value of count will be reset to 0 if reset is 1, otherwise, it will keep increasing until it reaches to 15, and will restart counting from 0.



III. 25k frequency divider(divb25kHz)

A. Verilog Code and Comment

```

1 module divb25kHz(clkin, reset, clkout);
2
3 input clkin, reset;
4 output reg clkout;
5 reg [31:0] count;
6 wire [31:0] divn, divnh;
7
8 assign divn= 32'd2000; //define divn to be 50M/25k = 2000
9 assign divnh= divn>>1; //define divnh to be half of divn
10
11 always@(posedge clkin) //while clkin is in posedge
12 begin
13     if((count>=divn)|| (reset)) //if counter is larger than the specified period of time
14         count<=1; //restart the counter
15     else
16         count<=count+1; //otherwise keep counting
17 end
18
19 always@(negedge clkin) //while clkin is in negedge
20 clkout= (count<= divnh)?1:0;
21 //output of the frequency divider is 1 while counting from 1 to the half period, otherwise is 0
22
23 endmodule


```

B. Simulation

We replace the frequency division ratio 32'd2000 into 32'd4 in order to make the simulation better be seen.

```
assign divn= 32'd4; //here, to simulate, we set the frequency of this divider into 1/4 of the input
assign divnh= divn>>1; //define divnh to be half of divn
```

 After modifying, we generate a frequency divider that can convert the input frequency into $1/4$ times of the frequency.



When `clkin` is in `posedge`, the value of `count` will be varied, while if `reset` is 1 at this moment, then 1 will be assigned into `count`.

When `clkin` is in `negedge`, `clkout` will compare the value of

count and the set value divnh, and output the correspond signal.

IV. fDiv (i frequency divider)

A. Verilog Code and Comment


```

1 module fDiv(fin,DivN, reset,fout);
2   input fin, reset;
3   output fout;
4   input [31:0]DivN; //the output value of DivNSel will be sent to the 32-bit input DivN
5   wire [31:0]_DivN; //define 32-bit wire _DivN
6   reg [31:0] count; //define 32-bit register count
7   reg fout; //define a register fout
8
9
10  assign _DivN = {1'b0,DivN[31:1]}; //_DivN = DivN/2
11
12  always@(posedge fin) //triggered at the positive edge of fin
13  begin
14    if(reset)
15      count<=32'd1; //when reset is 1, 32'd1 will be assigned into count
16    else
17      count<=(count>=DivN)?32'd1:count+1; //if count>=DivN, count=1 in decimal. if not, count=count+1
18      fout<=(count<=_DivN)?1'b0:1'b1; //if count<=_DivN, fout=0 in binary. if not fout=1 in binary
19  end
20 endmodule

```

 B. Simulation

The value of DivN is the output of the DivNSel, we can modified our frequency by simply changing the input frequency.



The operation of output signal and reset both happens when fin is in posedge, this is the reason why when the input signals change, there is a slice of delay in output.

V. Division Selector (DivNSel)

A. Verilog Code and Comment


```

1 module DivNSel(sel, DivN);
2   input [1:0] sel; //define a 2-bit input sel
3   output reg [31:0] DivN; //define a 32-bit output DivN
4
5   always@(sel)
6   begin
7     case(sel)
8       2'b00: DivN <= 32'd25000000; //when sel=00 in binary, we will make a 2Hz frequency divider
9       2'b01: DivN <= 32'd12500000; //when sel=01 in binary, we will make a 4Hz frequency divider
10      2'b10: DivN <= 32'd8333333; //when sel=10 in binary, we will make a 6Hz frequency divider
11      default: DivN <= 32'd6250000; //when sel is other value, we will make a 8Hz frequency divider
12    endcase
13  end
14 endmodule

```

 B. Simulation

The output value of DivN is depended on the input value of sel.




VI. One Shot

A. Verilog Code and Comment

```
1 module one_shot(clk,clk_i,s);
2   input clk,clk_i;
3   output reg s;
4   reg [1:0] cs,ns;
5   wire _s;
6
7   always @(posedge clk) //triggered when clk is in posedge
8     cs<=ns; //assign ns to cs
9
10  always @(cs) //when the value of cs differs, followed by the value of cs, we have following conditions
11  case(cs)
12    2'b00: ns <= (clk_i)?2'b01:2'b00; //if clk_i=1, assign 2'b01 to ns, else assign 2'b00 to ns
13    2'b01: ns <= 2'b10; //assign 2'b10 to ns
14    2'b10: ns <= (clk_i)?2'b10:2'b00; //if clk_i=1, assign 2'b10 to ns, else assign 2'b00 to ns
15    default: ns <= 2'b00; //otherwise, assign 2'b00 to ns
16  endcase
17
18  always @(posedge clk)
19    s <= _s;
20  assign _s = (cs==2'b01)?1'b1:1'b0; //if cs equals to 2'b01, s will be 1'b1, else it will be 1'b0
21
22 endmodule
```

 B. Simulation

The input of clk is the output of 25kHz frequency divider, while the input of clk_i is the output of changeable frequency divider. When clk is in posedge, one_shot will judge the value of clk_i, and assign the value of cs corresponding to the states. After that, the value of s would be assigned corresponding to the status of cs.




VII. Serial Out

A. Verilog Code and Comment

```
1 module serial_out(clk,Din,start,D);
2   input clk,start;
3   input [15:0] Din;
4   output D;
5   reg [15:0] Buf;
6   wire [15:0] nBuf;
7
8   assign nBuf= {Buf[14:0],Buf[15]}; //rotate left, the 16th bit will be the 1st bit
9   assign D=Buf[15]; //the output D is the last bit of Buf
10
11  always @(posedge clk)
12    if(start)
13      Buf <= Din; //if start=1, the value of Buf will be the input Din
14    else
15      Buf <= nBuf; // else it will rotate left
16
17 endmodule
```

 B. Simulation

When clk is in posedge with start =1, output the largest bit of current register Buf, else when clk is in posedge but start=0, rotate left the current register and output its largest bit.



VIII. Control

A. Verilog Code and Comment


```
1 module control (rst, clk_25k, start, str);
2   input rst, clk_25k;
3   output reg start, str;
4   reg [3:0] count;
5   wire _start, _str;
6
7   assign _start = ~(count); //if count is 4'b0000, _start = 1, else _start=0
8   assign _str = &count; //if count is 4'b1111, _str=1, else _str=0
9
10  always@ (posedge clk_25k) //triggered when clk_25k is posedge
11  begin
12    count <= (rst==1'b1)?4'd1:count+1; //if rst is 1'b1, assign 4'd1 to count, else count+1
13    str <= _str; //assign _str to output str
14    start <= _start; //assign _start to output start
15  end
16 endmodule
```

B. Simulation

In every posedge clk_25k, count will keep counting until rst is 1'b1, and the value of str and start will be assign at this moment too.

When count is 4'b0000, the value of start will be 1, and when count is 4'b1111, the value of str will be 1, in other case, they are 0.

 We know that after 1111, count will be 0000 again, that is the reason why after str=1, start will be 1 too.



IX. Reflection

The practical part of the experiment required us to solder circuits, a task I found a bit tricky and felt like it took up time and resources without a clear need. Even though the first time soldering circuit boards was kind of fun, thinking about future experiments involving soldering made me a bit tired, especially remembering the five hours we spent on it last time.

Moreover, the experiment guide didn't come with any ready-to-use code. This meant we had to tweak our existing modules, which was a bit tough. However, it turned out to be a good chance to improve our skills.