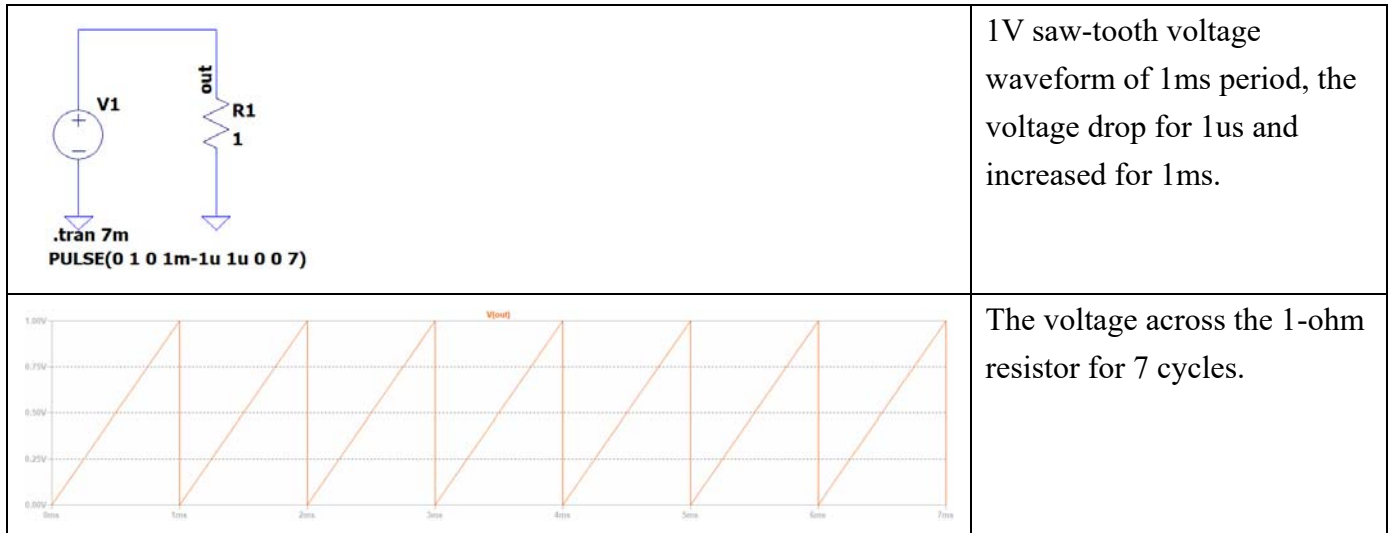



1.6.


Using the PULSE source statement of LTSpice, together with the circuit setup shown in Fig.P1.3, generate the saw-tooth voltage waveform shown in Fig. P1.6. Verify your results by plotting the voltage across the 1-ohm resistor for at least 6 cycles of its waveform.



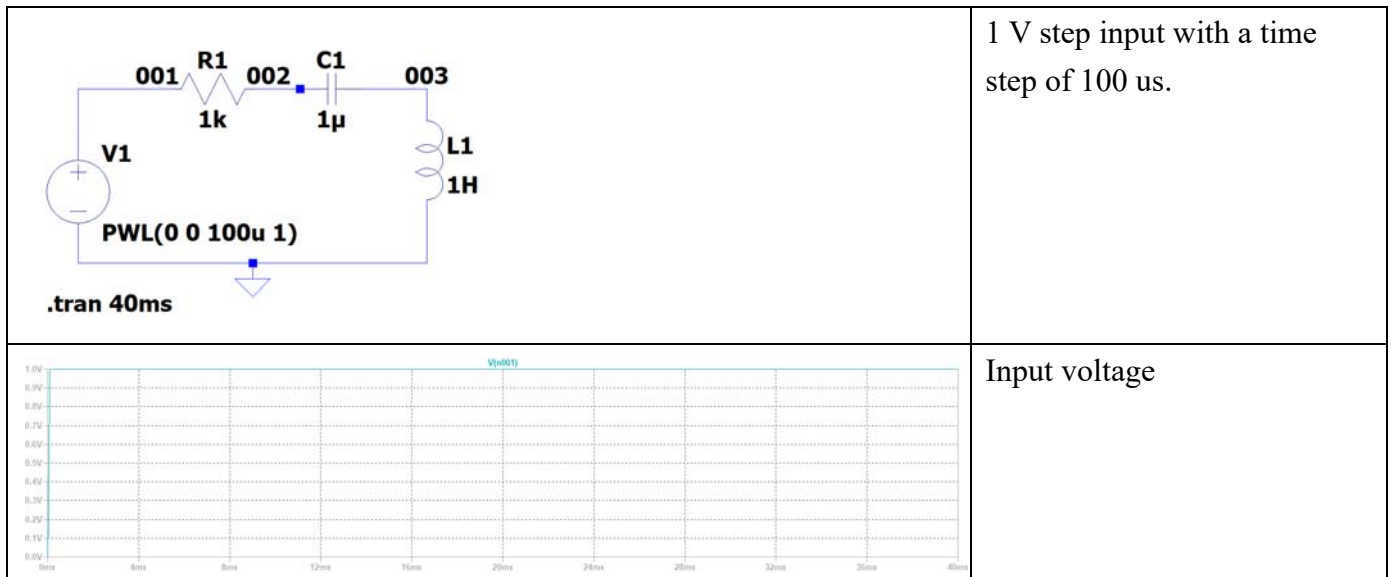1.17.

For the second order RLC circuit shown in Fig. P1.17 subject to a 1 V step input, simulate the transient behavior of the circuit and plot the voltage waveform that appears across each element for about 40 ms. Use a time step of no more than 100 us.



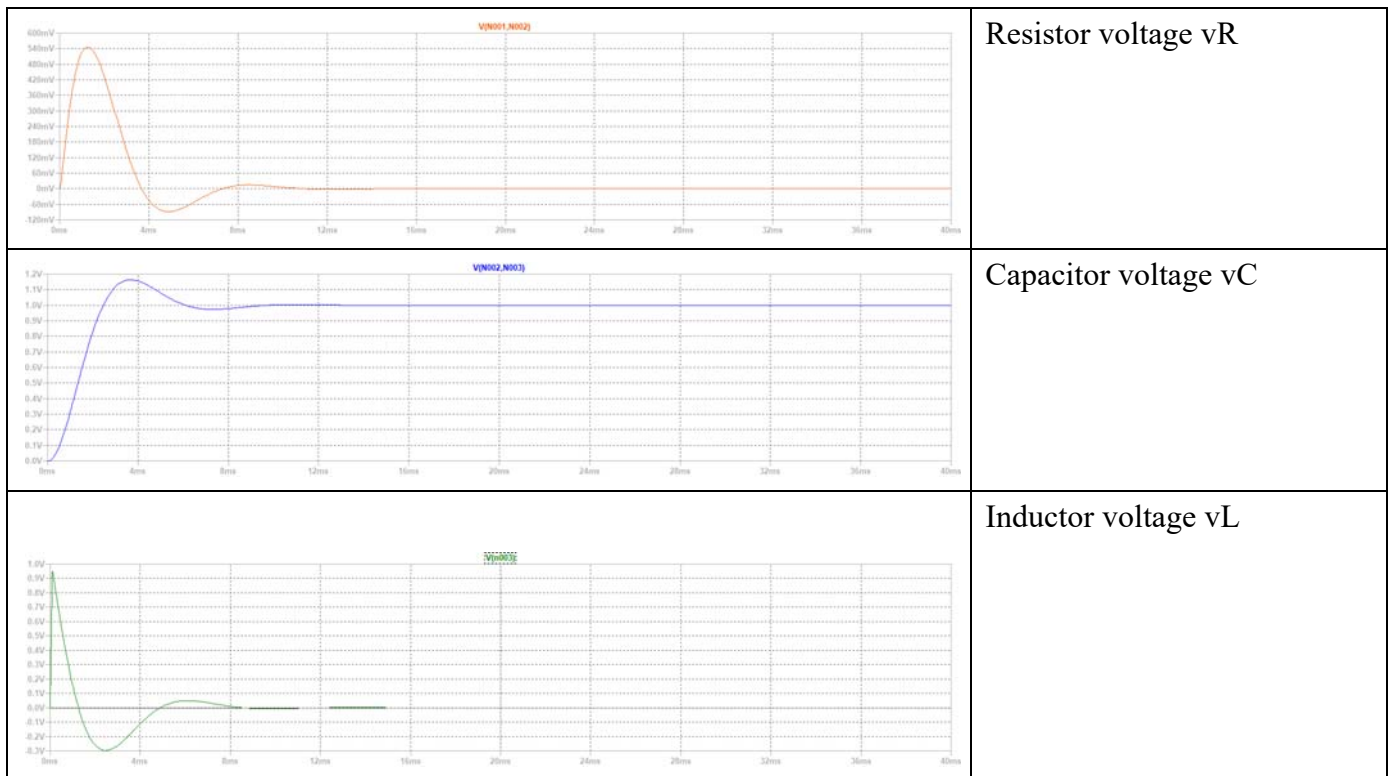


1.23.

Compute the frequency response behavior of the RLC circuit shown in Fig.P1.17 with R having values of 10, 100 and 1 k-ohm.

Plot the magnitude and phase response of each case and compare them. Select an appropriate frequency range and number of points that best illustrate your results.



Frequency range: (1,30k) ; Number of points: 100

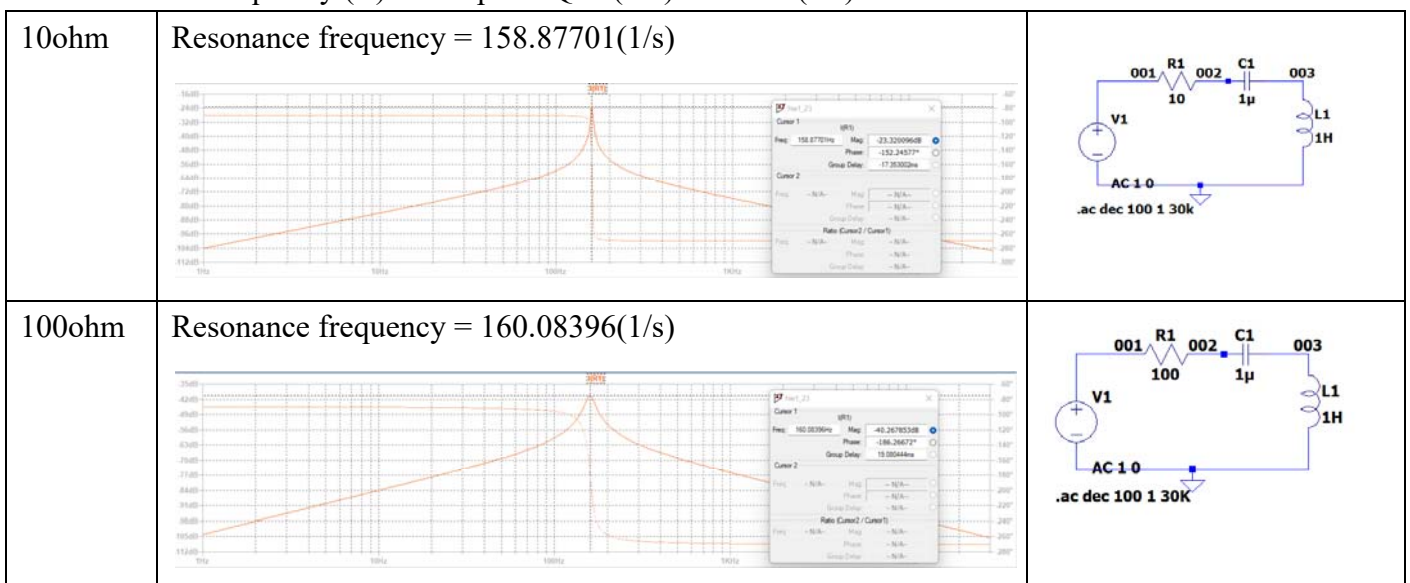Resonance frequency (f_r) = $1/2 \cdot \pi \cdot \sqrt{LC}$ = 159.15(1/s)



1kohm

Resonance frequency = 161.28082(1/s)

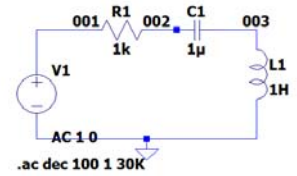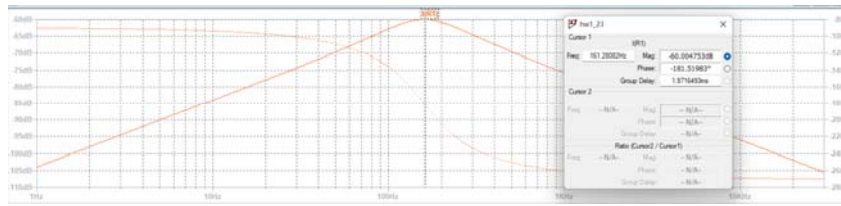

Reflection

This is our first time using LTSpice, I found it hard to conduct and simulate circuit, so I spent a lot of time reviewing and search for information; however, LTSpice is indeed really useful to present and simulate the experiment result. There are still lots of places for us to be familiar with, and I believe that those tools in LTSpice will help me a lot in the future, too.